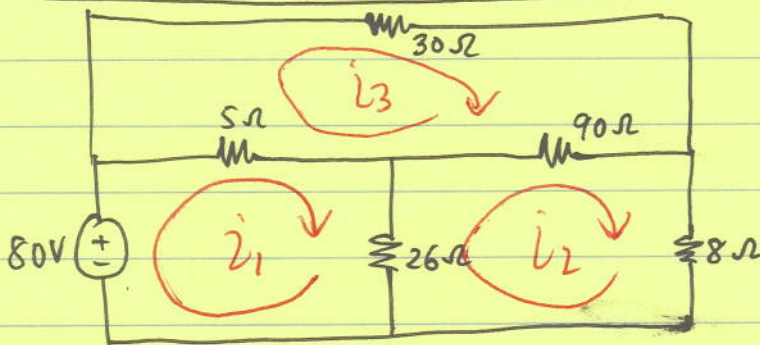


Mesh Current Method

- ① Draw a clockwise arrow inside every mesh.
- ② Label each arrow i_1, i_2, i_3, \dots
- ③ Check for special cases (see later)
- ④ Apply KVL around each mesh
- ⑤ Solve resulting equations for i_1, i_2, i_3, \dots

Ex



Find $\begin{cases} \text{mesh currents} \\ P_{\text{source}}, P_{8\Omega} \end{cases}$

$$\text{Mesh ①: } -80 + 5(i_1 - i_3) + 26(i_1 - i_2) = 0$$

$$\text{Mesh ②: } 26(i_2 - i_1) + 90(i_2 - i_3) + 8i_2 = 0$$

$$\text{Mesh ③: } 5(i_3 - i_1) + 30i_3 + 90(i_3 - i_2) = 0$$

$$\text{Std form: } i_1(5+26) + i_2(-26) + i_3(-5) = 80$$

$$i_1(-26) + i_2(26+90+8) + i_3(-90) = 0$$

$$i_1(-5) + i_2(-90) + i_3(5+30+90) = 0$$

$$\Rightarrow i_1 = 5A$$


$$i_2 = 2.5A$$

$$i_3 = 2A$$

$$P_{\text{source}} = 80V \times 5A = 400W$$

$$P_{8\Omega} = (2.5A)^2 \times 8\Omega = 50W$$

Ex

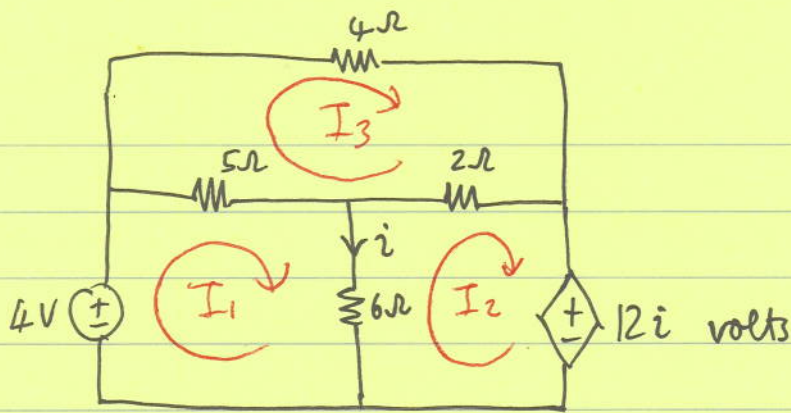

$$\text{mesh ①} : -4 + 5(I_1 - I_3) + 6(I_1 - I_2) = 0 \quad \dots \text{①}$$

$$\text{mesh ②} : 6(I_2 - I_1) + 2(I_2 - I_3) + 12i = 0 \quad \dots \text{②}$$

$$\text{mesh ③} : 4I_3 + 2(I_3 - I_2) + 5(I_3 - I_1) = 0 \quad \dots \text{③}$$

But $i = I_1 - I_2$, subst in ②:

$$6(I_2 - I_1) + 2(I_2 - I_3) + 12(I_1 - I_2) = 0 \quad \dots \text{②}'$$

Std form: $I_1(5+6) + I_2(-6) + I_3(-5) = +4$

$$I_1(-6+12) + I_2(2-12) + I_3(-2) = 0$$

$$I_1(-5) + I_2(-2) + I_3(4+2+5) = 0$$

$$I_1(11) + I_2(-6) + I_3(-5) = 4$$

$$I_1(6) + I_2(-4) + I_3(-2) = 0$$

$$I_1(-5) + I_2(-2) + I_3(11) = 0$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 11 & -6 & -5 \\ 6 & -4 & -2 \\ -5 & -2 & 11 \end{bmatrix}^{-1} \times \begin{bmatrix} 4 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 6A \\ 7A \\ 4A \end{bmatrix}$$

or use calculator
or Cramer's
method.

matrix inverse


Mesh Current Special Cases

Any current source will always cause a special case.

Case ①: Current source at outside edge of circuit
⇒ Known Mesh Current.

Case ②: Current source inside circuit
⇒ Supermesh

Case ① Known Mesh Current

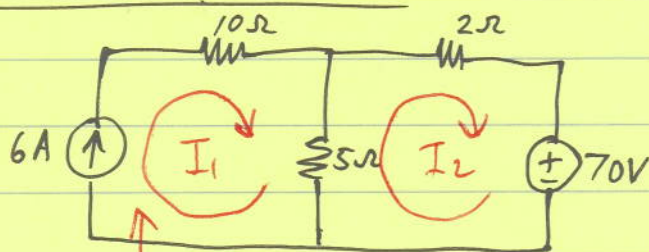

Special case: I_1 is known


$$\text{loop ① : } I_1 = 6$$

$$\text{loop ② : } 5(I_2 - I_1) + 2I_2 + 70 = 0$$

$$\text{Std form : } \begin{cases} I_1(1) + I_2(0) = 6 \\ I_1(-5) + I_2(5+2) = -70 \end{cases}$$

$$\Rightarrow \begin{cases} I_1 = 6 \text{ A} \\ I_2 = -5.714 \text{ A} \end{cases}$$

Ex

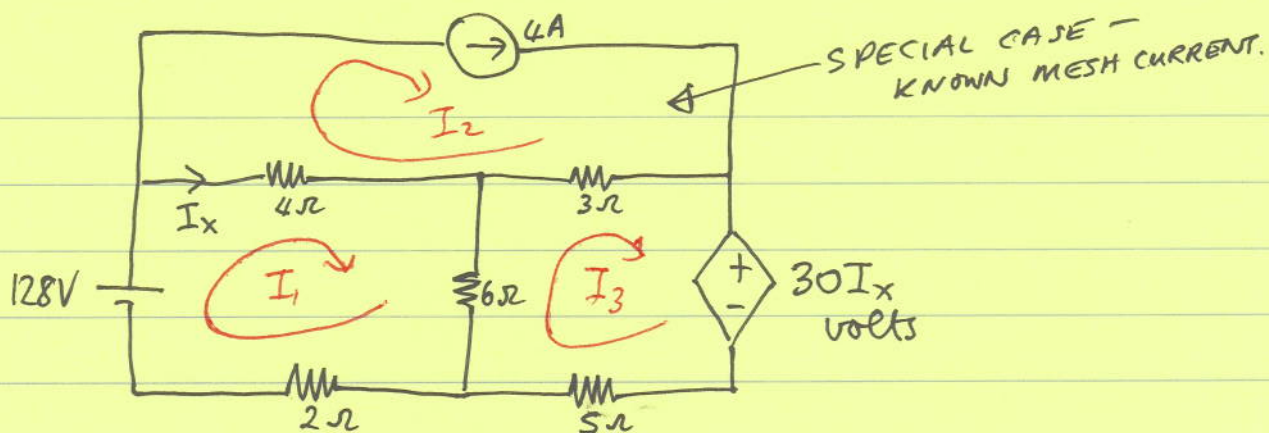

mesh ①: $-128 + 4(I_1 - I_2) + 6(I_1 - I_3) + 2I_1 = 0$

① mesh ②: $I_2 = 4$

mesh ③: $5I_3 + 6(I_3 - I_1) + 3(I_3 - I_2) + 30I_x = 0$

But $I_x = I_1 - I_2$

③': $5I_3 + 6(I_3 - I_1) + 3(I_3 - I_2) + 30(I_1 - I_2) = 0$


Std form:
$$\begin{cases} I_1(4+6+2) + I_2(-4) + I_3(-6) = +128 \\ I_1(0) + I_2(1) + I_3(0) = 4 \\ I_1(-6+30) + I_2(-3-30) + I_3(5+6+3) = 0 \end{cases}$$

$\Rightarrow I_1 = 9A$

$I_2 = 4A$

$I_3 = -6A$

Case (2): SUPERMESH

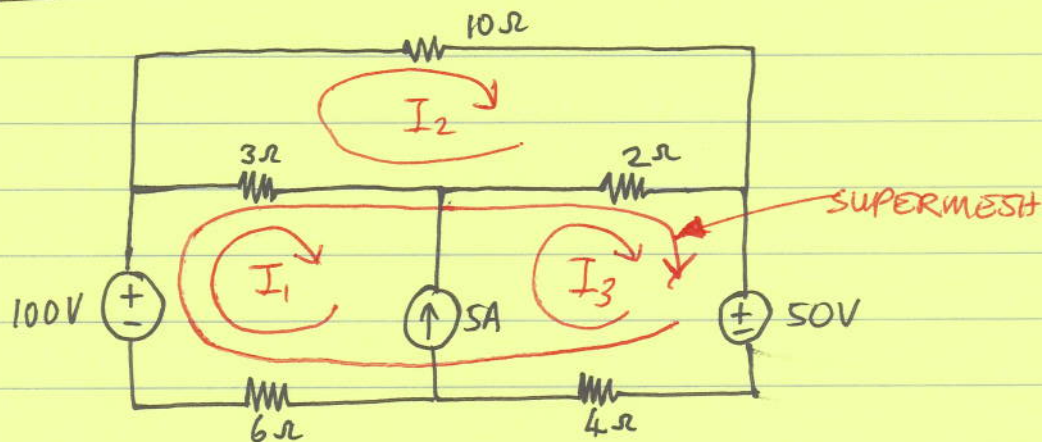

Current source ~~is~~ inside circuit \Rightarrow SUPERMESH.

Combine both meshes plus the current source into a supermesh.

$$\text{Mesh (2)} : 3(I_2 - I_1) + 10 \cdot I_2 + 2(I_2 - I_3) = 0$$

$$\text{Supermesh} : \begin{cases} -100 + 3(I_1 - I_2) + 2(I_3 - I_2) + 50 + 4I_3 + 6I_1 = 0 \\ I_3 - I_1 = 5 \quad \leftarrow \text{for the current source} \end{cases}$$

$$\text{Std form} : I_1(-3) + I_2(3+10+2) + I_3(-2) = 0$$

$$I_1(3+6) + I_2(-3-2) + I_3(2+4) = 100-50$$

$$I_1(-1) + I_2(0) + I_3(1) = 5$$

$$\Rightarrow I_1 = 1.75 \text{ A}$$

$$I_2 = 1.25 \text{ A}$$

$$I_3 = 6.75 \text{ A}$$