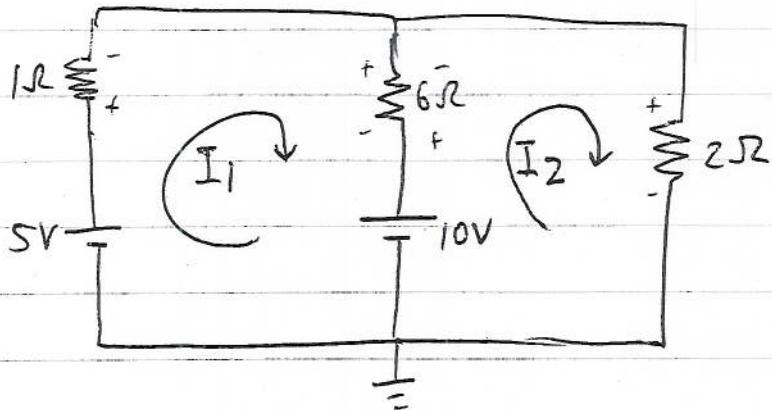


TI 89 +
92 +

TI Voyage 200

EX 8.12



$$\text{KVL : } \begin{cases} -5 + I_1 1 + (I_1 - I_2) 6 + 10 = 0 \\ ① \end{cases}$$


$$\text{KVL : } \begin{cases} -10 + (I_2 - I_1) 6 + I_2 2 = 0 \\ ② \end{cases}$$

$$\Rightarrow \begin{cases} I_1(7) + I_2(-6) = -5 \\ I_1(-6) + I_2(6+2) = +10 \end{cases}$$

$$\text{"Simult" } \Rightarrow \begin{cases} I_1 = 1A \\ I_2 = 2A \end{cases}$$

ON Simult $\frac{[I_1]}{New}$ solve = FS.

Ex 8.17

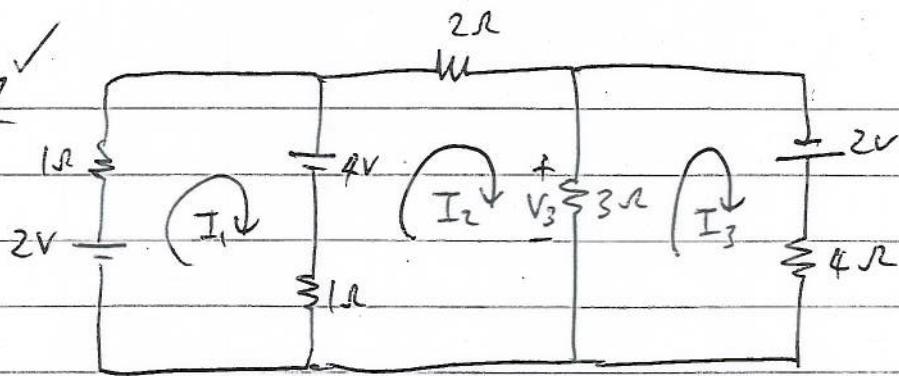

$$\text{loop ①: } -2 + I_1 1 + 4 + (I_1 - I_2) 1 = 0$$

$$\text{loop ②: } (I_2 - I_1) 1 - 4 + I_2 2 + (I_2 - I_3) 3 = 0$$

$$\text{loop ③: } (I_3 - I_2) 3 - 2 + I_3 4 = 0$$

$$\Rightarrow \begin{cases} I_1(1+1) + I_2(-1) + I_3(0) = -2 \\ I_1(-1) + I_2(1+2+3) + I_3(-3) = 4 \\ I_1(0) + I_2(-3) + I_3(3+4) = 2 \end{cases}$$


$$\stackrel{\text{simult}}{\Rightarrow} I_1 = -0.542$$

$$I_2 = 0.915$$

$$I_3 = 0.678$$

$$\text{Voltage } V_3 = (I_2 - I_3) 3 = 0.711 \text{ V}$$

Ex 8.20

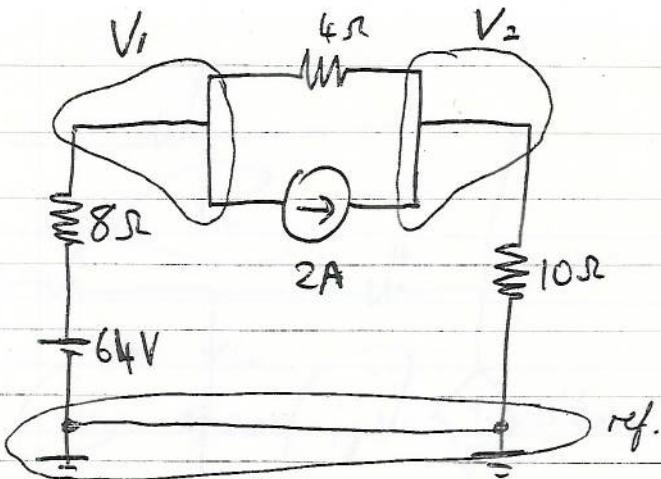


$$\left\{ \begin{array}{l} \text{Node ①: } \frac{V_1 - 64}{8} + \frac{V_1 - V_2}{4} + 2 = 0 \\ \text{Node ②: } \frac{V_2 - V_1}{4} + (-2) + \frac{V_2}{10} = 0 \end{array} \right.$$

$$\Rightarrow \left\{ \begin{array}{l} V_1 \left(\frac{1}{8} + \frac{1}{4} \right) + V_2 \left(-\frac{1}{4} \right) = \underbrace{-2 + 8}_6 \\ V_1 \left(-\frac{1}{4} \right) + V_2 \left(\frac{1}{4} + \frac{1}{10} \right) = 2 \end{array} \right.$$

Simul
 $\Rightarrow \left\{ \begin{array}{l} V_1 = 37.818V \\ V_2 = 32.727V \end{array} \right.$

Node voltage

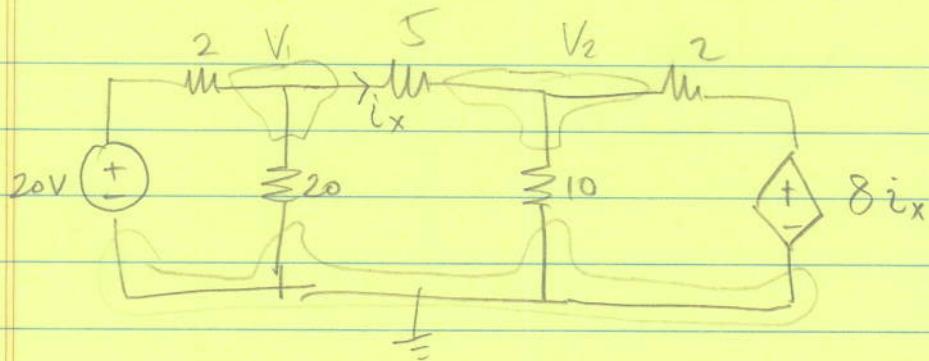

$$\frac{V_1 - 20}{2} + \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{5} = 0 \quad \textcircled{1}$$

$$\frac{V_2 - V_1}{5} + \frac{V_2 - 0}{10} + \frac{V_2 - 8i_x}{2} = 0 \quad \textcircled{2}$$

But $i_x = \frac{V_1 - V_2}{5}$ (Ohm's law)

$$\frac{V_2 - V_1}{5} + \frac{V_2 - 0}{10} + \frac{V_2 - 8\left(\frac{V_1 - V_2}{5}\right)}{2} = 0 \quad \textcircled{1}'$$

OR $\left\{ V_1 \left(\frac{1}{2} + \frac{1}{20} + \frac{1}{5} \right) + V_2 \left(-\frac{1}{2} \right) = +\frac{20}{2} \right.$


$$\left. V_1 \left(-\frac{1}{2} - \frac{8}{5 \times 2} \right) + V_2 \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{2} + \frac{8}{5 \times 2} \right) = 0 \right.$$

$$\begin{bmatrix} 0.75 & -0.2 \\ -1 & 1.6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0.75 & -0.2 \\ -1 & 1.6 \end{bmatrix}^{-1} \begin{bmatrix} 10 \\ 0 \end{bmatrix} = \begin{bmatrix} 16 \\ 10 \end{bmatrix}$$

$$P_{5\Omega} = \frac{V^2}{R} = \frac{(V_2 - V_1)^2}{5} = \frac{(10 - 16)^2}{5} = \frac{36}{5} = 7.2W$$

Meth

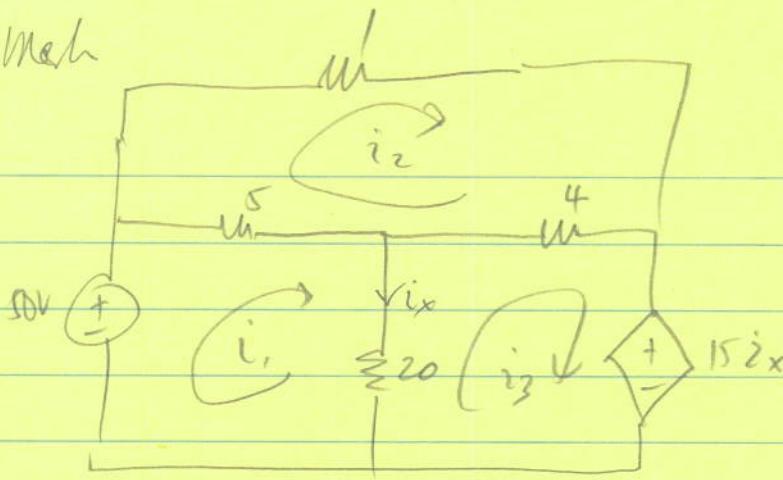

$$\text{loop ①} \quad -50 + 5(i_1 - i_2) + 20(i_1 - i_3) = 0 \quad \text{--- ①}$$

$$\text{②} \quad 20(i_3 - i_1) + 4(i_2 - i_1) + 15i_x = 0 \quad \text{--- ②}$$

$$\text{③} \quad 5(i_2 - i_1) + 1i_2 + 4(i_2 - i_3) = 0 \quad \text{--- ③}$$

But $i_x = i_1 - i_3$.

$$\text{②} \Rightarrow 20(i_3 - i_1) + 4(i_3 - i_2) + 15(i_1 - i_3) = 0.$$

$$\left\{ \begin{array}{l} i_1(5+20) + i_2(-5) + i_3(-20) = +50 \\ i_1(-20+15) + i_2(-4) + i_3(20+4-15) = 0, \\ i_1(-5) + i_2(-5+1+4) + i_3(-4) = 0 \end{array} \right.$$

$$i_1 = 29.6 \text{ A}$$

$$i_2 = 26 \text{ A}$$

$$i_3 = 28 \text{ A}$$