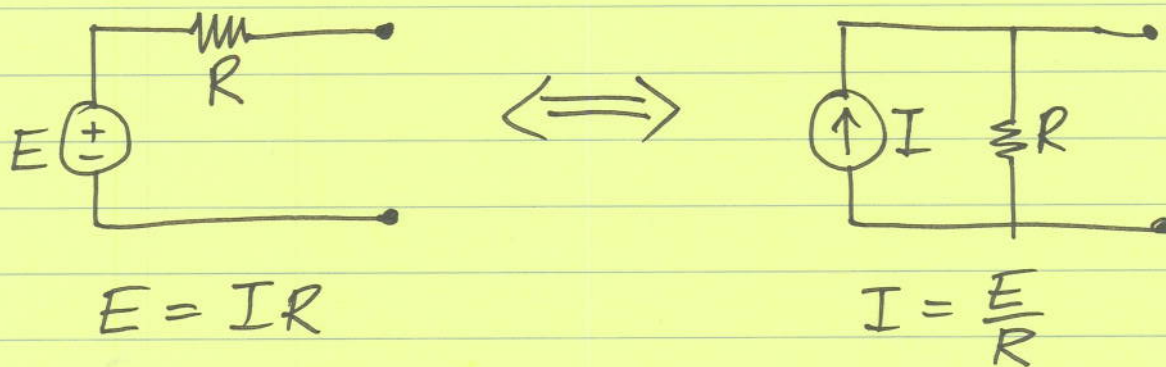



Source Transformations

Any voltage source that is connected in series with a resistor can be replaced by a current source in parallel with the same resistance.


Any current source that is connected in parallel with a resistor can be replaced by a voltage source in series with the same resistance.



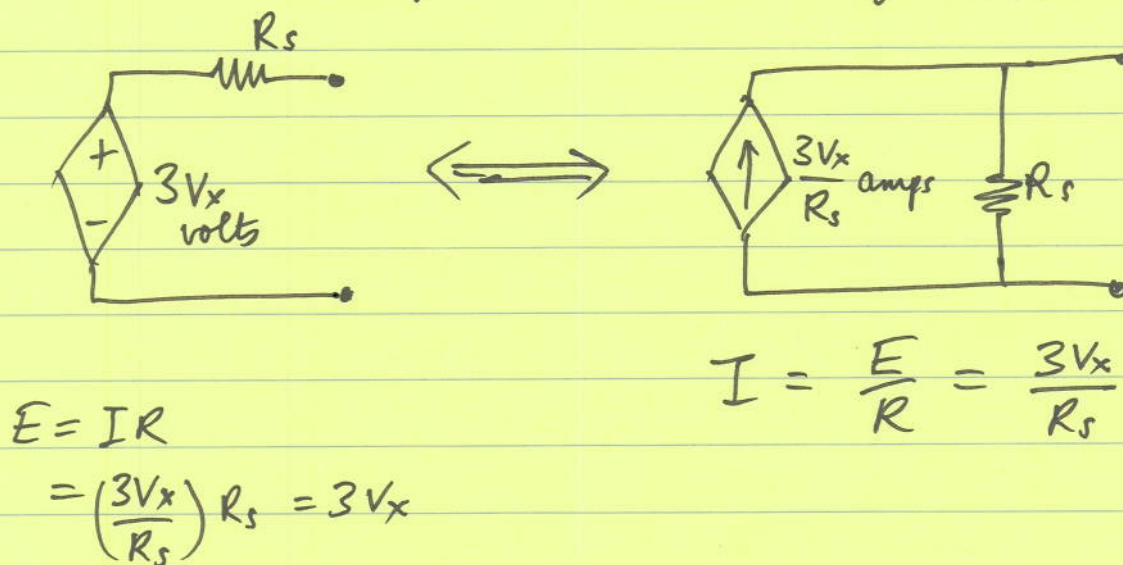Note: Source transformations also work for dependent sources:




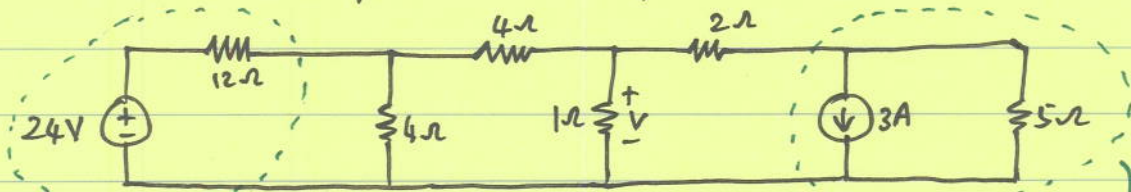Ex Use Source Transformations to find V :




$$V = (3A)5\Omega = 15V$$

ln: $I = \frac{24V}{12\Omega} = 2A$

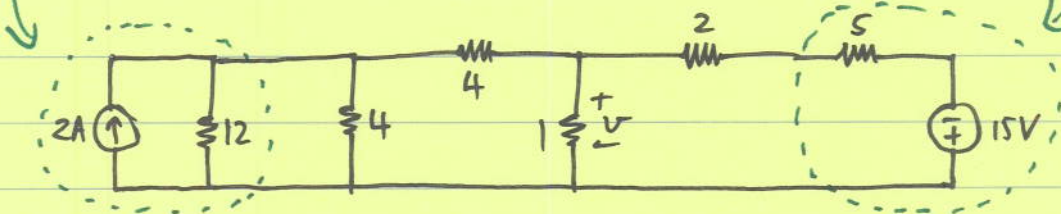


$$12\Omega \parallel 4\Omega = 3\Omega$$

$$2\Omega + 5\Omega = 7\Omega$$

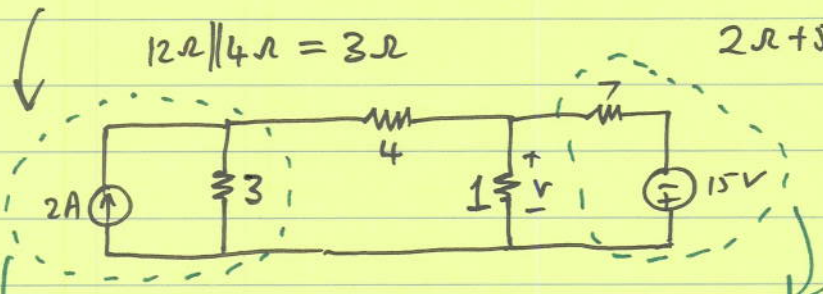


$$I = \frac{15V}{7\Omega} = 2.14286A$$


$$V = (2A)(3\Omega) = 6V$$

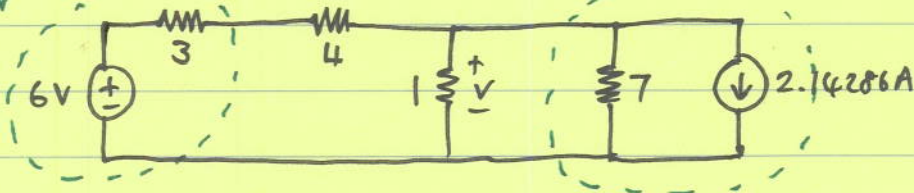

$$3 + 4 = 7\Omega$$

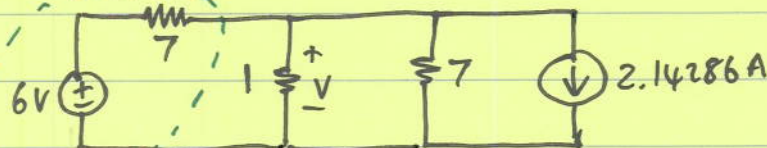


$$I = \frac{6}{7} = 0.85714A$$

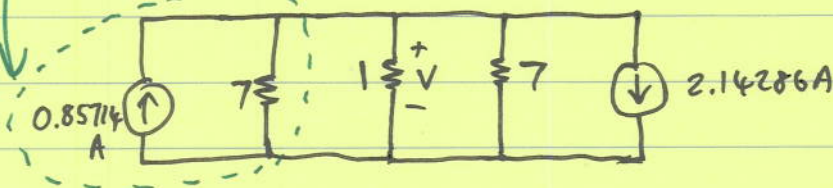

Now combine current sources: $0.85714A + (-2.14286A) = -1.28572A$

Combine the two 7Ω resistors: $7\Omega \parallel 7\Omega = 3.5\Omega$.

So circuit reduces to:

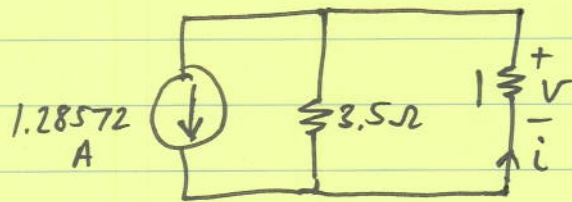

Get i using current divider: $i = 1.28572 \cdot \frac{3.5}{1+3.5}$

$$= -1\text{ A}.$$

So, $v = (-1\text{ A})(1\Omega) = -1\text{ V}$

This should be +1A

This is correct.