
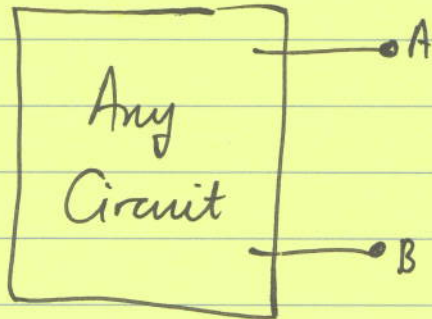

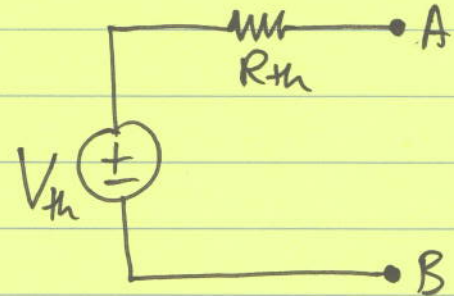
# Thevenin Equivalent Circuit

Any linear circuit with 2 terminals is equivalent to a voltage source in series with a resistance.



$\equiv$




THEVENIN EQUIVALENT

$V_{th}$  = Thevenin Voltage  
 $R_{th}$  = Thevenin Resistance

source transform
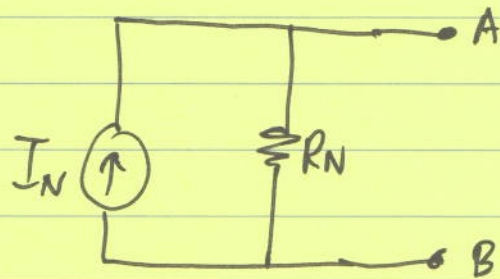
$$R_N = R_{th}$$
$$I_N = \frac{V_{th}}{R_{th}}$$



NORTON EQUIVALENT

2  
 $V_{th} = \text{open circuit voltage of circuit} = V_{oc}$

$I_N = \text{short circuit current of circuit} = I_{sc}$

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

How to find the Thevenin Voltage :

$V_{th} = \text{the open circuit voltage}$

So, draw circuit with nothing connected to A, B and then find  $V_{th} = \text{voltage between A \& B}$ .

How to find the Thevenin Resistance :

There are 3 methods :

$R_{th}$  method (A) : Equivalent resistance method


Suppress all independent sources, then  $R_T = \text{resistance looking into terminals (A, B)}$ .

(This is the easiest method - use when circuit has no dependent sources)

3
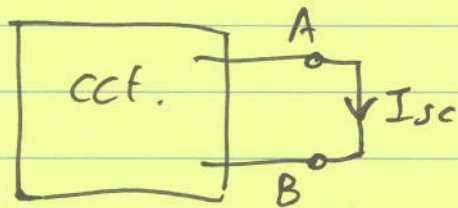
## R<sub>th</sub> method (B) : Short-circuit current method


Draw the circuit with a short across A & B and then find I<sub>sc</sub>.



$$\text{Then } R_{th} = \frac{V_{th}}{I_{sc}}$$

(use when circuit has both dependent and independent sources)
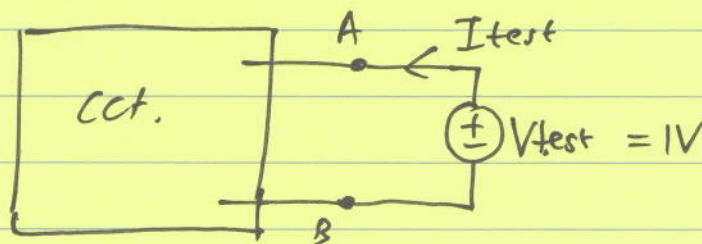
## R<sub>th</sub> method (C) : Test Source Method




Attach a test source to A & B., then  $R_{th} = \frac{V_{test}}{I_{test}}$ .

(this method works for any circuit, but is much more work than method (A))

(use when all sources are dependent).

Ex Find Thevenin equivalent of:

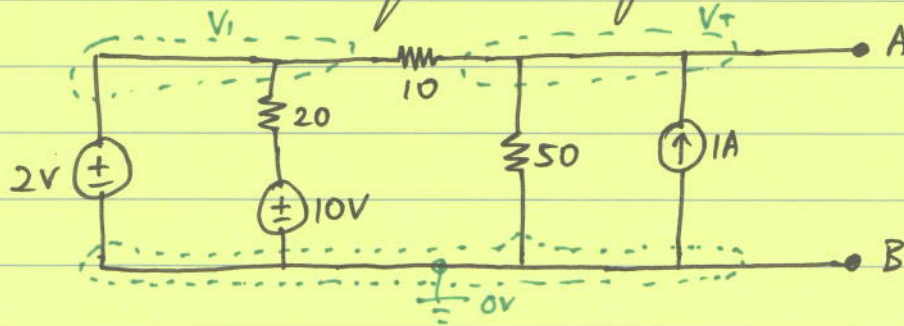

V<sub>th</sub>:  $V_1 = 2V$  (KNOWN NODE VOLTAGE special case)


$$\frac{V_T - V_1}{10} + \frac{V_T - 0}{50} + (-1) + 0 = 0$$

$$\Rightarrow \frac{V_T - 2}{10} + \frac{V_T}{50} - 1 = 0$$


$$\Rightarrow V_T \left( \frac{1}{10} + \frac{1}{50} \right) = 1 + \frac{2}{10}$$

$$\Rightarrow V_T = 1.2 / 0.12 = 10V$$


R<sub>th</sub>: use method (A)

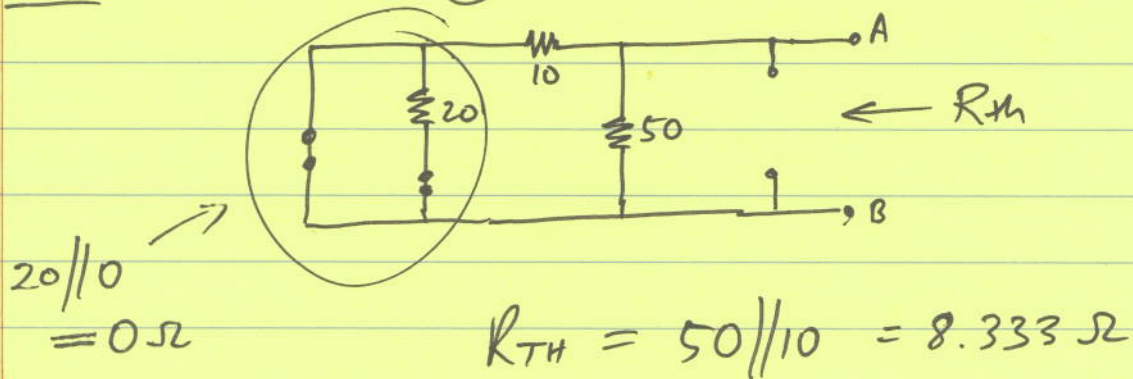


Thevenin equiv. is

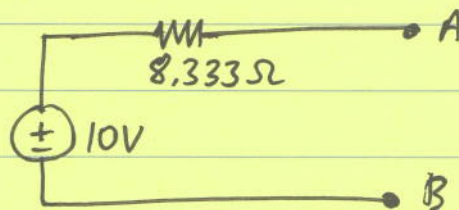

Ex Find Thev. Equiv. of:

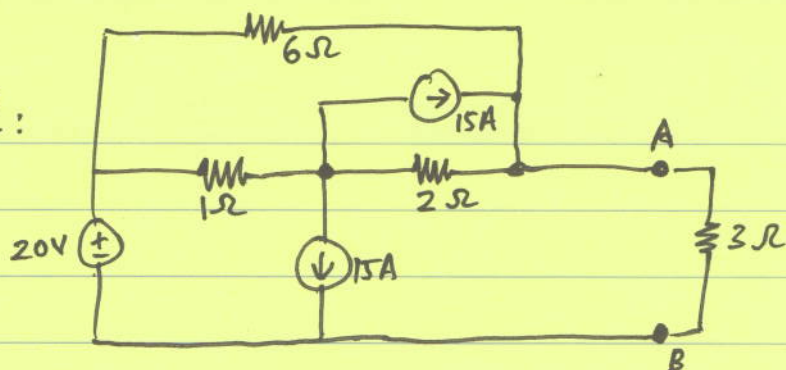

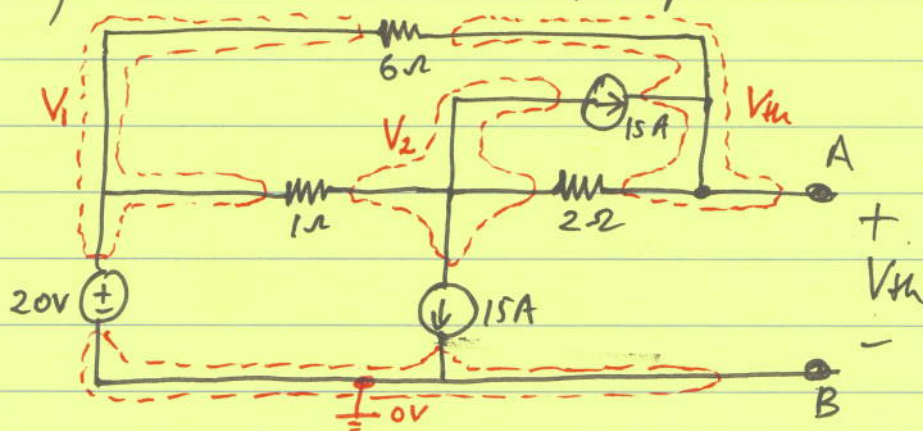Soln For  $V_{th}$ , draw circuit with (A,B) open-circuit:



Special case: Known node voltage  $V_1 = 20V$ .

Node 1:  $V_1 = 20$

Node 2:  $\frac{V_2 - V_1}{1} + 15 + \frac{V_2 - V_{th}}{2} + 15 = 0$

Node  $V_{th}$ :  $\frac{V_{th} - V_1}{6} + (-15) + \frac{V_{th} - V_2}{2} + 0 = 0$


Standard form: 
$$\begin{cases} V_1(1) + V_2(0) + V_{th}(0) = 20 \\ V_1(-1) + V_2(1 + \frac{1}{2}) + V_{th}(-\frac{1}{2}) = -30 \\ V_1(-\frac{1}{6}) + V_2(-\frac{1}{2}) + V_{th}(\frac{1}{6} + \frac{1}{2}) = +15 \end{cases}$$

$$\Rightarrow \begin{aligned} V_1 &= 20V \\ V_2 &= 3.3333V \\ V_{th} &= 30V \end{aligned}$$

Now get  $R_{th}$ :


For  $R_{th}$  : No dependent sources  $\Rightarrow$  Method A will work.

Suppress all independent sources :

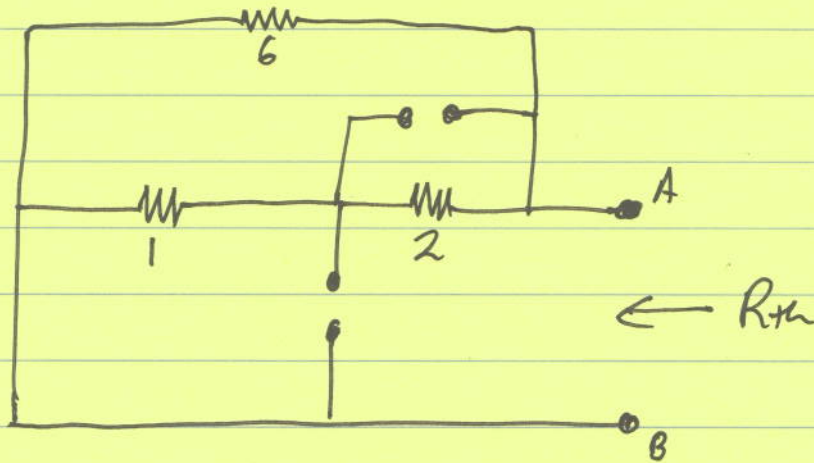


$$R_{th} = (1+2) \parallel 6 = 3 \parallel 6$$
$$= \frac{3 \times 6}{3+6} = 2 \Omega$$


So, Thev. equiv. circuit is :

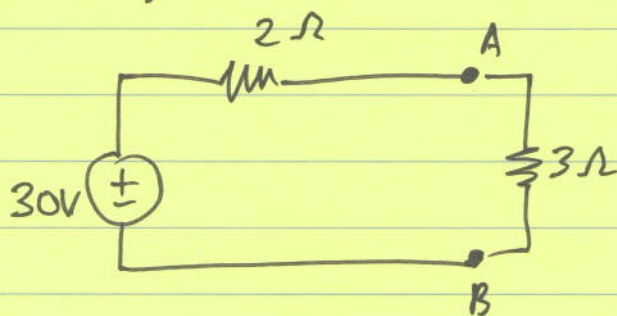

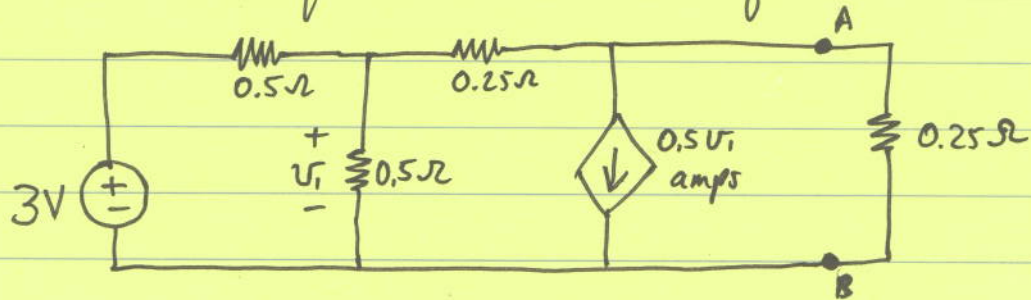7  
Ex Find Thevenin equivalent circuit of:



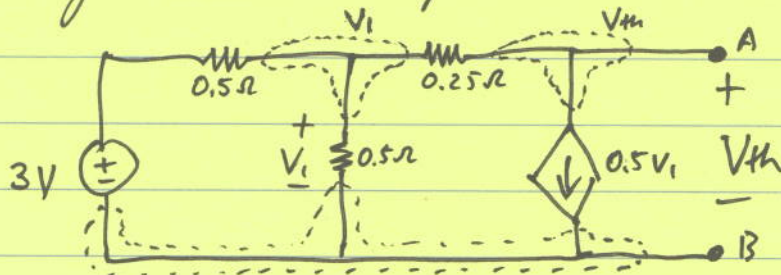Soln: First get  $V_{th}$  = open-circuit voltage:



$$\text{Node } V_1: \frac{V_1 - 3}{0.5} + \frac{V_1 - 0}{0.5} + \frac{V_1 - V_{th}}{0.25} = 0$$

$$\text{Node } V_{th}: \frac{V_{th} - V_1}{0.25} + (0.5V_1) + 0 = 0$$

$$\text{Standard form: } \begin{cases} V_1 \left( \frac{1}{.5} + \frac{1}{.5} + \frac{1}{.25} \right) + V_{th} \left( -\frac{1}{.25} \right) = \frac{3}{.5} \\ V_1 \left( -\frac{1}{.25} + 0.5 \right) + V_{th} \left( \frac{1}{.25} \right) = 0 \end{cases}$$


$$\Rightarrow \begin{cases} V_1 (8) + V_{th} (-4) = 6 \\ V_1 (-3.5) + V_{th} (4) = 0 \end{cases}$$

$$\Rightarrow \begin{bmatrix} V_1 \\ V_{th} \end{bmatrix} = \begin{bmatrix} 8 & -4 \\ -3.5 & 4 \end{bmatrix}^{-1} \begin{bmatrix} 6 \\ 0 \end{bmatrix} = \begin{bmatrix} 1.3333 \text{ V} \\ 1.1667 \text{ V} \end{bmatrix}$$

$$V_{th} = 1.16667 \text{ V}$$

Now get  $R_{th}$ :

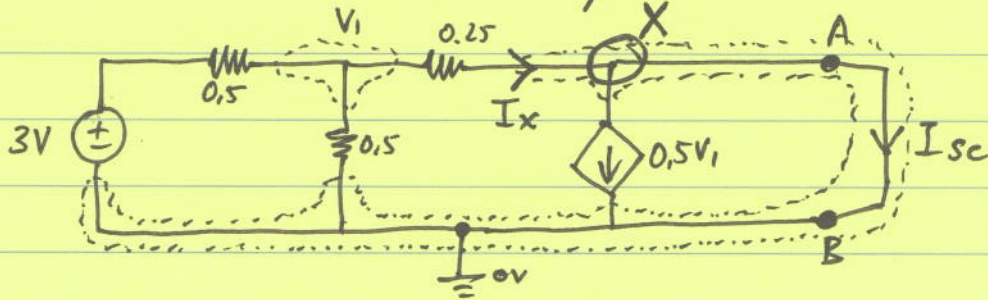For  $R_{th}$ : Circuit has a dependent source so use method (B):



Node  $V_1$ :  $\frac{V_1 - 3}{0.5} + \frac{V_1 - 0}{0.5} + \frac{V_1 - 0}{0.25} = 0$

$$\Rightarrow V_1 \left( \frac{1}{0.5} + \frac{1}{0.5} + \frac{1}{0.25} \right) = \frac{3}{0.5}$$

$$\Rightarrow V_1 (2 + 2 + 4) = 6$$

$$\Rightarrow V_1 = 6/8 = 0.75 \text{ V}$$

KCL:  $(-I_x) + (0.5V_1) + I_{sc} = 0$

(X)

But  $I_x = \frac{V_1 - 0}{0.25} = \frac{0.75}{0.25} = 3 \text{ A}$  (ohm's law)

and  $0.5V_1 = 0.5(0.75) = 0.375 \text{ A}$


$$\Rightarrow (-3) + (0.375) + I_{sc} = 0$$

$$\Rightarrow I_{sc} = 3 - 0.375 = 2.625 \text{ A}$$

$$R_{th} = \frac{V_{th}}{I_{sc}} = \frac{0.75 \text{ V}}{2.625 \text{ A}} = 0.4444 \Omega$$


Correction: should be 1.16667V not 0.75V

Then equiv is:

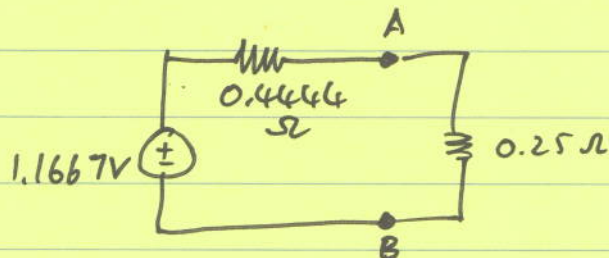




Ex Find Thev. Equivalent of

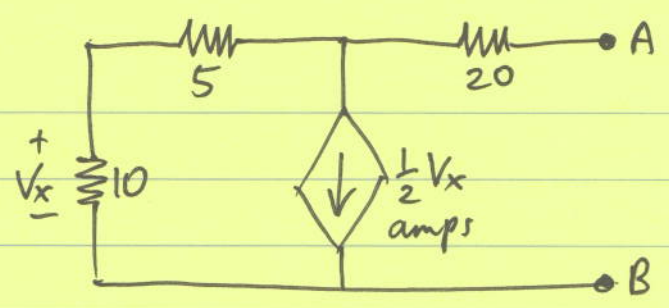

Soln:  $V_{th}$  = open circuit voltage = 0V since there is no independent voltage or current source.

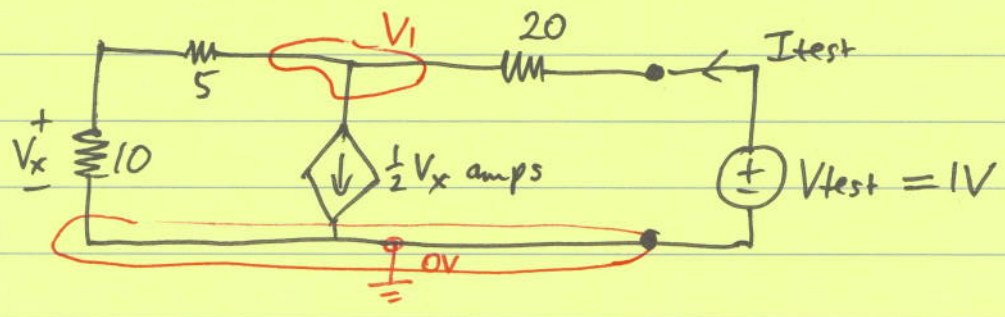R<sub>th</sub>: Will have to use Method (B):



Let  $V_{test} = 1V$ .

KCL :  $\frac{V_1 - 0}{15} + (\frac{1}{2}V_x) + \frac{V_1 - 1V}{20} = 0$   
 node (1)

But  $V_x = V_1 \cdot \frac{10}{10+5} = \frac{2}{3}V_1$  (voltage divider)

$\Rightarrow \frac{V_1}{15} + \frac{1}{2}(\frac{2}{3}V_1) + \frac{V_1 - 1}{20} = 0$

$\Rightarrow V_1 (\frac{1}{15} + \frac{1}{3} + \frac{1}{20}) = \frac{1}{20}$

$\Rightarrow V_1 = \frac{1}{20} / (\frac{1}{15} + \frac{1}{3} + \frac{1}{20}) = 0.111111V$

$\Rightarrow I_{test} = \frac{1V - 0.111111V}{20\Omega} = 0.044444A$

$\Rightarrow R_{th} = \frac{V_{test}}{I_{test}} = \frac{1V}{0.044444A} = 22.5\Omega$

