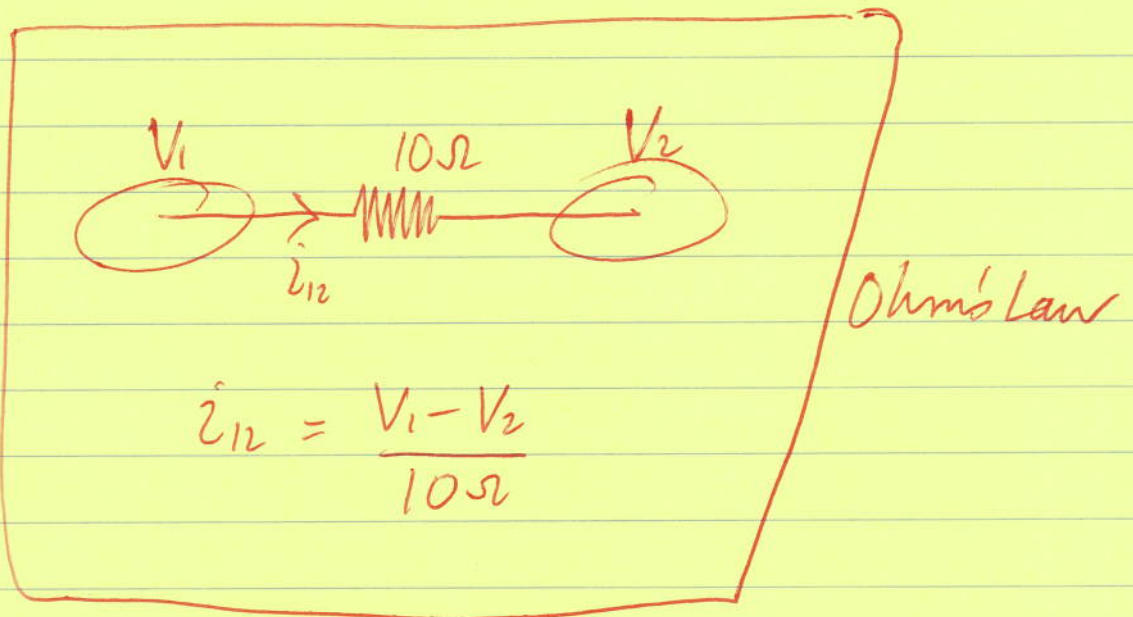


Node = a bunch of wire that joins 2 or more circuit elements together.


Nonessential node = a node that connects only 2 elements.
Essential node = a node that connects more than 2 elements.

Node Voltage Method

- ① Identify all essential nodes.
- ② Label one of them as "ground" = 0V.
- ③ Label the others with node voltages V_1, V_2, V_3, \dots
- ④ Check for special cases (see later)
- ⑤ Write KCL for each node.
- ⑥ Solve resulting eqns for V_1, V_2, V_3, \dots



Ex

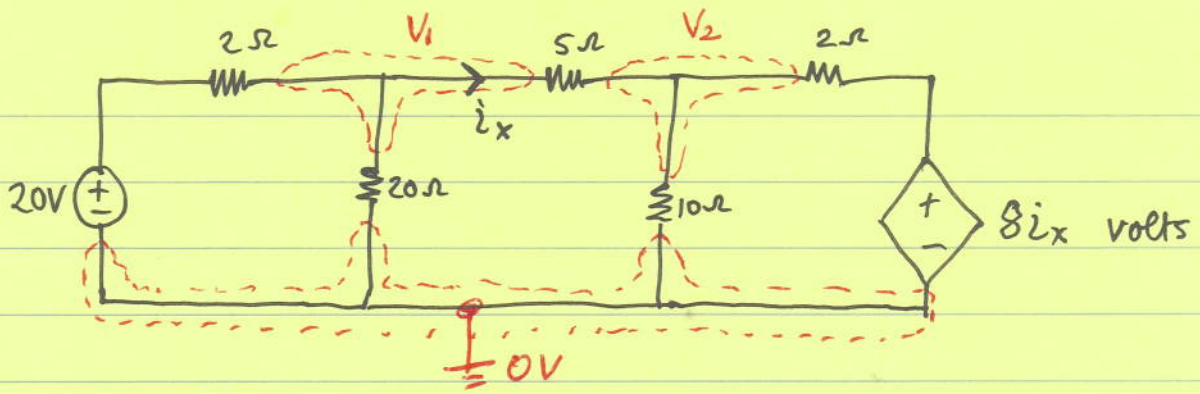

$$\text{Node } V_1: \frac{V_1 - 20}{2} + \frac{V_1 - 0}{20} + \frac{V_1 - V_2}{5} = 0 \quad \dots \textcircled{1}$$

$$\text{Node } V_2: \frac{V_2 - V_1}{5} + \frac{V_2 - 0}{10} + \frac{V_2 - 8i_x}{2} = 0 \quad \dots \textcircled{2}$$

But $i_x = \frac{V_1 - V_2}{5}$ (ohm's law). Subst. into $\textcircled{2}$.

$$\textcircled{2} \Rightarrow \frac{V_2 - V_1}{5} + \frac{V_2 - 0}{10} + \frac{V_2 - 8\left(\frac{V_1 - V_2}{5}\right)}{2} = 0 \quad \dots \textcircled{2}'$$

$$\text{Standard form } \begin{cases} V_1 \left(\frac{1}{2} + \frac{1}{20} + \frac{1}{5} \right) + V_2 \left(-\frac{1}{5} \right) = +\frac{20}{2} \\ V_1 \left(-\frac{1}{5} - \frac{8}{2 \times 5} \right) + V_2 \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{2} + \frac{8}{2 \times 5} \right) = 0 \end{cases}$$

Solve using calculator or Cramer's Rule

$$\Rightarrow \begin{cases} V_1 = 16V \\ V_2 = 10V \end{cases}$$

Node Voltage Special Cases


Case ①: Voltage source directly from ground to another node

⇒ Known Node Voltage

Case ②: Voltage source directly from one non-ground node to another

⇒ Supernode

CASE ① KNOWN NODE VOLTAGE

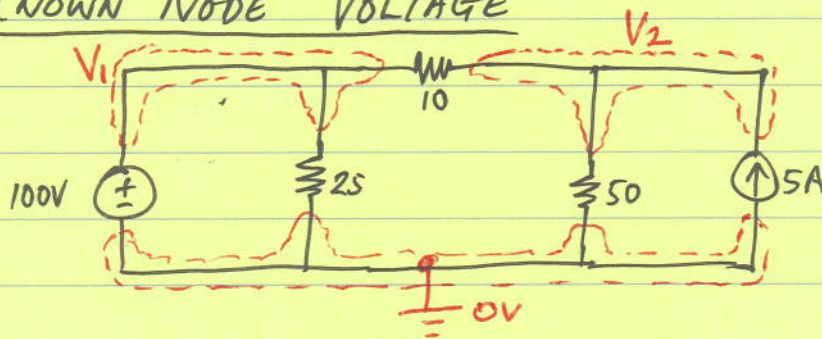

10V source directly from ground to V_1 ⇒ Known node voltage V_1 .

Ⓚ node 1 : $V_1 = 100V$


node 2 : $\frac{V_2 - V_1}{10} + \frac{V_2 - 0}{50} + (-5) = 0$

std. form : $V_1(1) + V_2(0) = 100$

$$V_1\left(-\frac{1}{10}\right) + V_2\left(\frac{1}{10} + \frac{1}{50}\right) = +5$$

$$\Rightarrow \begin{cases} V_1 = 100V \\ V_2 = 125V \end{cases}$$

CASE ② SUPERNODE

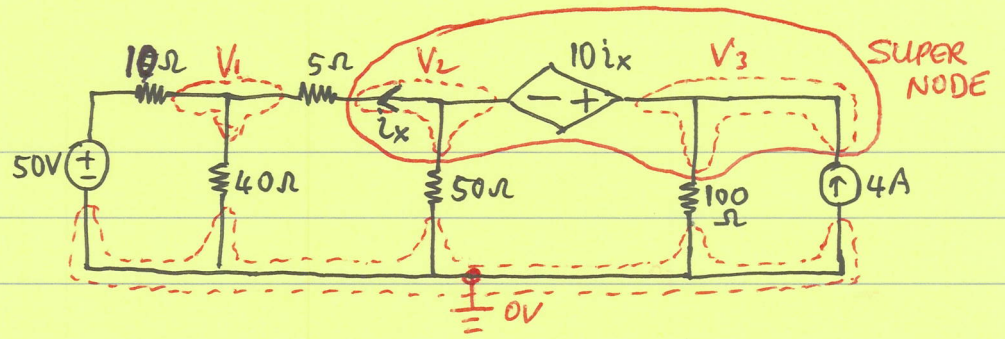

$10i_x$ voltage source is connected directly from node ② to node ③.
Form a SUPERNODE consisting of nodes ② & ③ and the voltage source.

$$\text{Node ①: } \frac{V_1 - 50}{10} + \frac{V_1 - 0}{40} + \frac{V_1 - V_2}{5} = 0 \quad \text{--- ①}$$

$$\text{Supernode: } \begin{cases} \frac{V_2 - V_1}{5} + \frac{V_2 - 0}{50} + \frac{V_3 - 0}{100} + (-4) = 0 & \text{--- ②} \\ V_3 - V_2 = 10i_x & \text{--- ③} \end{cases}$$

$$\text{But } i_x = \frac{V_2 - V_1}{5}$$

$$\Rightarrow V_3 - V_2 = 10 \left(\frac{V_2 - V_1}{5} \right)$$

$$\Rightarrow V_3 - V_2 = 2V_2 - 2V_1$$

$$\Rightarrow V_3 - 3V_2 + 2V_1 = 0 \quad \text{--- ③'}$$

$$\text{Std. form: } \begin{cases} V_1 \left(\frac{1}{10} + \frac{1}{40} + \frac{1}{5} \right) + V_2 \left(-\frac{1}{5} \right) + V_3 (0) = +\frac{50}{10} \\ V_1 \left(-\frac{1}{5} \right) + V_2 \left(\frac{1}{5} + \frac{1}{50} \right) + V_3 \left(\frac{1}{100} \right) = +4 \\ V_1 (2) + V_2 (-3) + V_3 (1) = 0 \end{cases}$$

$$\Rightarrow \begin{cases} V_1 = 55.03 \text{ V} \\ V_2 = 64.43 \text{ V} \\ V_3 = 83.22 \text{ V} \end{cases}$$