



Method of Superposition


If circuit has more than one independent source, then any voltage or current can be found by summing the responses due to each independent source acting alone.

"acting alone" \Rightarrow we need to know how to suppress independent sources

voltage source  \rightarrow  short.


current source  \rightarrow  open.

Ex Use superposition to find V and i :

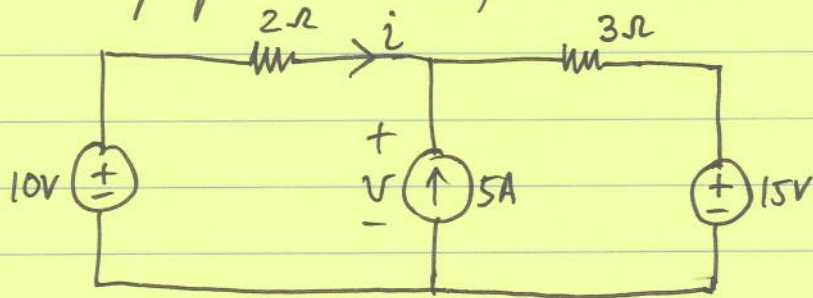

3 dependent sources so we make 3 circuits: ~~with~~


10V acting alone:

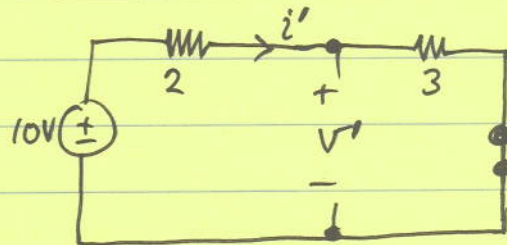

$$i' = \frac{10V}{2+3\Omega} = 2A$$

$$V' = 10V \times \frac{3}{3+2} = 6V \quad (\text{using voltage divider rule})$$

5A acting alone:

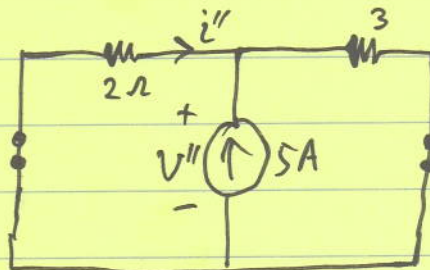


$$2\Omega \parallel 3\Omega = \frac{2 \times 3}{2+3} = 1.2\Omega$$

$$V'' = 5A \times 1.2\Omega = 6V$$

$$i'' = \frac{-6V}{2\Omega} = -3A$$

15V acting alone:

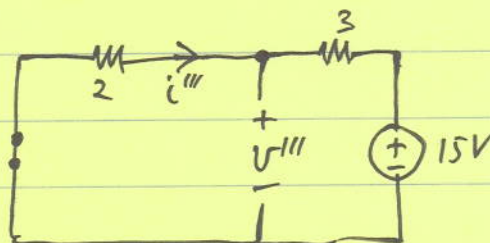

$$i''' = \frac{-15V}{2+3\Omega} = -3A$$


$$V''' = 3A \times 2\Omega = 6V$$

Add contributions $V = V' + V'' + V''' = 6 + 6 + 6 = 18V$

$$i = i' + i'' + i''' = 2 + (-3) + (-3) = -4A.$$

Unfortunately, dependent sources $\diamond \rightarrow$ $\diamond - +$ do not suppress:


Ex with a dependent source

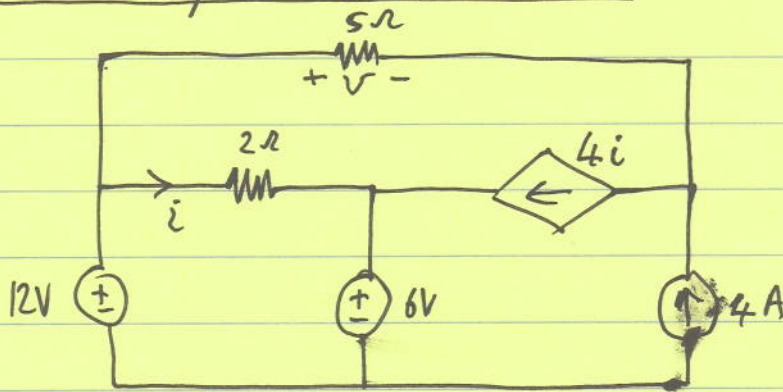


Find i & v
using superposition.

Soln

12V acting alone:

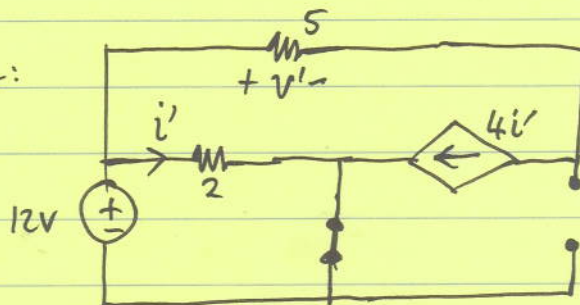

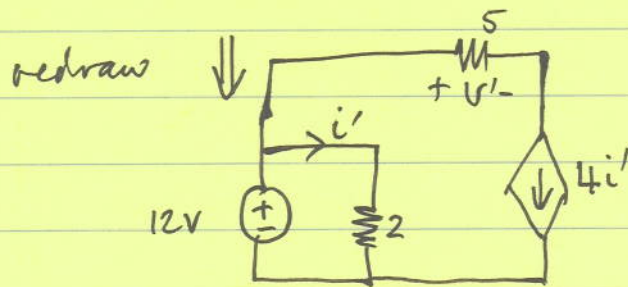Note the dependent source $4i'$ does not suppress!!




$$\Rightarrow i' = \frac{12V}{2\Omega} = 6A$$


$$v' = (4i')(5\Omega) \quad \text{ohm's law}$$

$$= 4 \times 6 \times 5 = 120V.$$

6V acting alone:

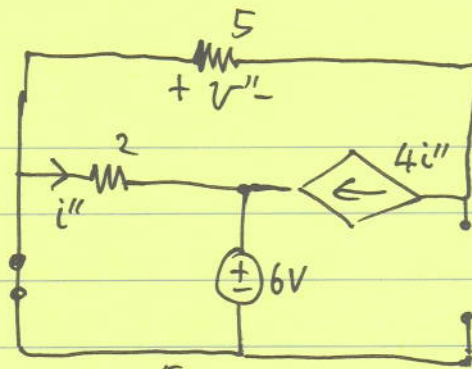

redraw ↴

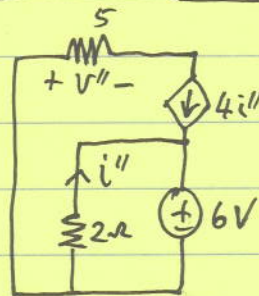


$$\Rightarrow i'' = -\frac{6V}{2\Omega} = -3A$$

$$v'' = (4i'')(5\Omega) \text{ ohm's law}$$

$$= 4(-3)5 = 60V$$

4A acting alone:

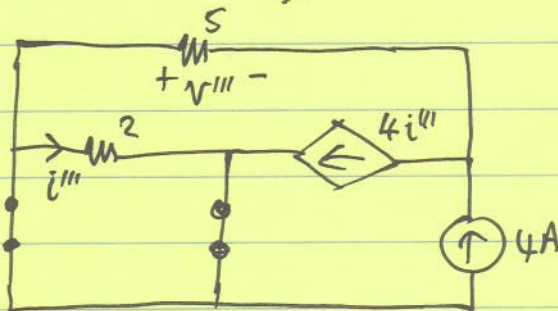

$$\text{Note: } 2\Omega \text{ is shorted} \Rightarrow i''' = \frac{0V}{2\Omega} = 0A$$

$$\Rightarrow 4i''' = 4 \times 0 = 0A$$

So all of the 4A passes thru the 5Ω

$$\Rightarrow v''' = -(4A)(5\Omega) = -20V.$$

Add contributions

$$v = v' + v'' + v''' = 120 + 60 + (-20) = 160V$$

$$i = i' + i'' + i''' = 6 + (-3) + 0 = 3A.$$