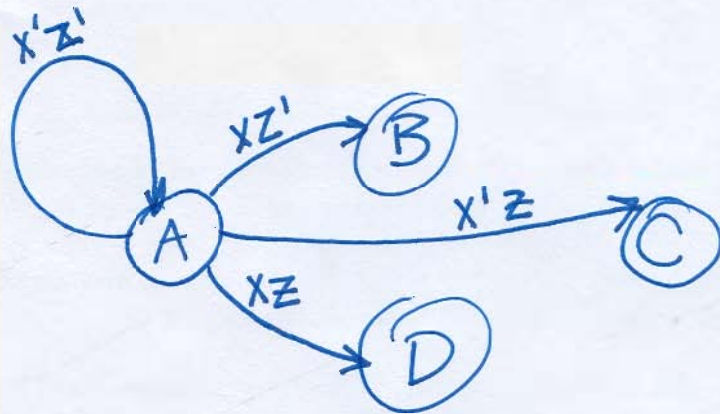


# ECOR 2181 Extra Notes - 12/1/08

①




For our "machine," we have inputs  $x, y, z$ . Go to state B if  $x=1$ , go to state C if  $z=1$ , remain in A otherwise. What if  $x=1$  and  $z=1$ ? In the case of  $x=1, z=1$ , go to state D.

$x y z$	next	
0 0 0	A	Identify if some transitions are missing or redundant.
0 0 1	C	
0 1 0	A	
0 1 1	C	
1 0 0	B	
1 0 1	D	
1 1 0	B	
1 1 1	D	

$a(r' + b + g)$  WAIT

(2)

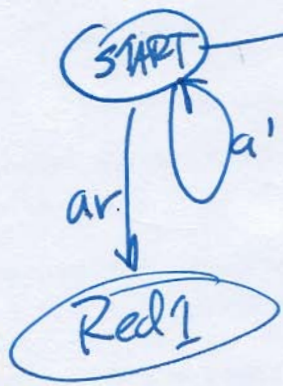

$ar' + ab + ag$

In a FSM, each set of inputs can cause you to go to only one next state

	a	r	b	g	
m0	0	0	0	0	START
m1	0	0	0	1	START
m2	0	0	1	0	ST
m3	0	0	1	1	ST
m4	0	1	0	0	ST
m5	0	1	0	1	ST
m6	0	1	1	0	ST
m7	0	1	1	1	ST
m8	1	0	0	0	WAIT
m9	1	0	0	1	WAIT
m10	1	0	1	0	WAIT
m11	1	0	1	1	WAIT
m12	1	1	0	0	Red1
m13	1	1	0	1	Red1 WAIT
m14	1	1	1	0	Red1 WAIT
m15	1	1	1	1	Red1 WAIT

Violation!!!

solution ar should be ar'b'g'

# ECGR 2181 - Extra Notes - 12/1/08

3

