

# Computer Assignment 2

ECGR 2181 - Fall 2009

## Assignment Overview

In this assignment you will use Xilinx ISE 7.1i and ModelSim to build and simulate an Arithmetic Logic Unit created from schematics and VHDL. The assignment is based on Homework 8. Refer to Homework 8 for the operations the ALU must be able to perform. Demo the final simulation to one of the TAs during their Office Hours (in Woodward 200). **You are allowed to work in groups of 2 as long as you are both in the same section.** Make sure you both understand everything, when you demo the final solution the TA will ask you both questions regarding the system to make sure you both did the work.

In addition you will need to upload a **single PDF** of the two schematics and two VHDL along with the Grade Rubric. Print each page to a PDF file and use Adobe Acrobat to combine the four pages to a single PDF. Name the PDF <lastname\_lastname\_cad2>.pdf (so schmidt\_conrad\_cad2.pdf). Upload the PDF to Moodle under Computer Assignment 2.

**The Computer Assignment is due Wednesday, November 4<sup>th</sup> by 3 PM.**

## Getting Started

1. Create a new directory to store all of the Computer Assignment Files
2. Open **Xilinx ISE 7.1i** and Create a New Project called: **computer\_assignment\_2**
3. Create it for the **Nexys2 Board** (Spartan 3E, xc3s500e, fg320, -4)
4. Add 1 New Source File called of type VHDL: **my\_alu\_vhdl**
  - a. **This will be the top level design for your Arithmetic Logic Unit. At the end we will describe what code is necessary in this file. For now simply set the Input and Output ports to the following:**

Port Name	Direction	MSB	LSB
a	in	7	0
b	in	7	0
op	in	2	0
sum	out	7	0
overflow	out		
	in		

5. Click Next / Finish to complete the New Project Wizard

## Full Adder

### 1. 1-Bit Full Adder

- Add a New Source of type Schematic to the project: **full\_adder\_1\_bit\_sch**
- Create a schematic of a 1-bit full adder from gates. Look at the Chapter 4 notes if you are not sure how to get started.
- Inputs: A, B, Cin
- Outputs: S, Cout
- Save the schematic and under the Process View for the full\_adder\_1\_bit\_sch expand Design Utilities to select and run **Create Schematic Symbol**. This creates the schematic symbol that you will need for part 2 below.

### 2. 8-Bit Full Adder (full\_adder\_8\_bit\_sch)

- Add a New Source of type Schematic to the project: **full\_adder\_8\_bit\_sch**
- Using the full\_adder\_1\_bit\_sch created above create an 8-bit cascaded Full Adder.
- In addition to the Full Adder circuit, add the logic needed for Overflow calculation. Look at the Chapter 4 notes if you are not sure how to calculate the Overflow.
- Inputs: A(7:0), B(7:0), Cin
- Outputs: S(7:0), Cout, Overflow
- Save the schematic. It is recommended (although not required) to simulate the 8-bit Full Adder at this point. Good engineering practice is to test components as they are built making the debugging easier as the design becomes more complex.

## Multiplexer with VHDL

### 1. 8-bit 8 to 1 Multiplexer

- Add a New Source of type VHDL Module to the project: **mux\_8\_to\_1\_8\_bit\_vhdl**
- Set the Input and Output ports to the following:

Port Name	Direction	MSB	LSB
i0	in	7	0
i1	in	7	0
i2	in	7	0
i3	in	7	0
i4	in	7	0
i5	in	7	0
i6	in	7	0
i7	in	7	0
s	in	2	0
f	out	7	0
	in		
	in		
	in		

- Select Finish.
- This opens a new VHDL template file which already has some of the code we need.

- e. At Line 47 (between “**begin**” and “**end Behavioral;**”) create a VHDL Process. This process will set the output “**f**” to the input (i0, i1, i2... i7) based on the value of “**s**”. A VHDL process is similar to a function in C++, except when the inputs change the output will automatically change as well.

```

47     output_process : process (s, i0, i1, i2, i3, i4, i5, i6, i7) is
48     begin
49         case (s) is
50             when "000" => f <= i0;
51             when "001" => f <= i1;
52             when "010" => f <= i2;
53             when "011" => f <= i3;
54             when "100" => f <= i4;
55             when "101" => f <= i5;
56             when "110" => f <= i6;
57             when "111" => f <= i7;
58             when others => f <= (others => '0');
59         end case;
60     end process output_process;

```

- f. The process is named: **output\_process**
- g. The Sensitivity List (the inputs to the process) are: **s, i0, i1, i2, i3, i4, i5, i6, i7**
- h. The output “**f**” is set to the corresponding input.
- i. For example when s = “011” f is assigned the value of i3.
- Save the VHDL file and in the Process View select “**Synthesis – XST**”. If there are any syntax errors, fix them and re-synthesize until a green check mark appears.
  - It is recommended (although not required) to simulate the 8-bit Mux at this point.

## My ALU

- Open **my\_alu\_vhdl** file in Xilinx ISE 7.1i (it was the first file you created when you started this project). You will now use VHDL to connect the Multiplexer and Adder together along with the correct Carry-In logic you designed from Homework 8 to complete the ALU. You will also need to look at Homework 8 to see which Inputs are needed for the 8 to 1 Multiplexer. We will provide you with a nearly complete template; you need to connect the correct signals together for the fully functional ALU circuit.
- At line 39 add the following:

```

39     -- Temporary 8 Bit Signals for A and B Inverted
40     signal a_inv : std_logic_vector(7 downto 0);
41     signal b_inv : std_logic_vector(7 downto 0);
42
43     -- Intermediate Value for Mux Output to Adder Input
44     signal mux_out : std_logic_vector(7 downto 0);
45
46     -- Intermediate Value for Adder's Initial Cin
47     signal adder_cin : std_logic;
48
49     -- Intermediate Value for Adder's Carry Out
50     signal adder_cout : std_logic;
51

```

- These signals are like “wires” and “buses” in the schematics you have designed. Instead of connecting components together with the wires, we will use VHDL signals (similar to variables in C++). You will start to see the simplicity of using a Hardware Description Language to quickly and concisely create complex systems.
- Next at line 52 add the following:

```

52  -- Declare 8 Bit 8:1 Mux
53  component mux_8_1_8_bit_vhdl is
54      Port ( i0 : in  std_logic_vector(7 downto 0);
55             i1 : in  std_logic_vector(7 downto 0);
56             i2 : in  std_logic_vector(7 downto 0);
57             i3 : in  std_logic_vector(7 downto 0);
58             i4 : in  std_logic_vector(7 downto 0);
59             i5 : in  std_logic_vector(7 downto 0);
60             i6 : in  std_logic_vector(7 downto 0);
61             i7 : in  std_logic_vector(7 downto 0);
62             s  : in  std_logic_vector(2 downto 0);
63             f  : out std_logic_vector(7 downto 0));
64  end component mux_8_1_8_bit_vhdl;
65
66  -- Declare 8 Bit Full Adder
67  component full_adder_8_bit_sch is
68      Port ( a   : in  std_logic_vector(7 downto 0);
69            b   : in  std_logic_vector(7 downto 0);
70            cin : in  std_logic;
71            s   : out std_logic_vector(7 downto 0);
72            cout : out std_logic;
73            overflow : out std_logic);
74  end component full_adder_8_bit_sch;

```

5. These are Component Declarations. They tell the VHDL file what components are going to be used within this circuit. Here we are going to use the 8-bit 8 to 1 Multiplexer and the 8-bit Full Adder that you created earlier.
6. The body of the VHDL code is provided below. This template is missing a few parts which you will need to fill in:

```

78  -- Invert A and B
79  a_inv <= not(a);
80  b_inv <= not(b);
81
82  -- Adder Cin Value based on KMAP Reduction
83  adder_cin <= ;
84
85  -- Instantiate 8-Bit Mux
86  mux_i : mux_8_1_8_bit_vhdl
87      Port Map (
88          i0 => b,
89          i1 => b_inv,
90          i2 => ,
91          i3 => ,
92          i4 => ,
93          i5 => ,
94          i6 => ,
95          i7 => ,
96          s  => op,
97          f  => mux_out);
98
99  -- Instantiate 8-Bit Adder
100  adder_i : full_adder_8_bit_sch
101      Port Map (
102          A   => ,
103          B   => mux_out,
104          cin => adder_cin,
105          s   => ,
106          cout => ,
107          overflow => overflow);

```



### Required Electronic Submission (uploaded to Moodle)

Print the Grading Rubric (the last page of this hangout) and write both names and section number at the top. Then print the two schematics and two VHDL files listed below as individual PDFs (make sure to add both names and section number as text to each schematic and as comments in the VHDL). Combine the four PDFs into a single PDF with both your last names as the filename (I.E. schmidt\_conrad\_ca2.pdf). Upload the single PDF (one upload per group) to Moodle. Finally, find one of the TAs **during their Office Hours** and demo the outputs of both ModelSim simulations.

1. Schematic of 1-Bit Full Adder
2. Schematic of 8-Bit Full Adder
3. VHDL of 8-bit 8 to 1 Multiplexer
4. VHDL of My ALU

### Notes

You do NOT need to checkout a Nexys2 Board for this Computer Assignment. You are only using the software tools to build and test the designs. Future assignments will rely upon these components so make sure to keep a copy of your project's directory.

If you run into a License Error during Simulation save all files and close Xilinx ISE 7.1i. The open Xilinx ISE 7.1i from the Start Menu:

Start -> Mosaic XP -> Engineering -> Electrical -> Xilinx Webpack -> Xilinx ISE 7.1i

If you run into a ModelSim "read only" error on your Test Bench VHW file:

- a. To avoid getting any errors with ModelSim in "read mode" you MUST create a new project directory WITHOUT any spaces! Make sure the path to the directory also does not have any spaces. If you are not sure where to save this project to, create the following directory on your desktop:
  - i. ecgr2181
  - ii. Then within this directory add a new directory for each project
  - iii. The Path to this directory will now be: **U:\pc\win\_data\Desktop\ecgr2181**

## Computer Assignment #2 - Grading Rubric

Student 1 Name: \_\_\_\_\_

Section Number: \_\_\_\_\_

Student 2 Name: \_\_\_\_\_

### Uploaded schematics and VHDL as a Single PDF to Moddle:

- Schematic of 1-Bit Full Adder \_\_\_\_\_ / 3 Points
- Schematic of 8-Bit Full Adder \_\_\_\_\_ / 4 Points
- VHDL of 8-bit 8 to 1 Multiplexer \_\_\_\_\_ / 3 Points
- VHDL of My ALU \_\_\_\_\_ / 7 Points

### Demo of the simulations:

- Simulation of ALU in ModelSim \_\_\_\_\_ / 8 Points

**Total** \_\_\_\_\_ / 25 Points