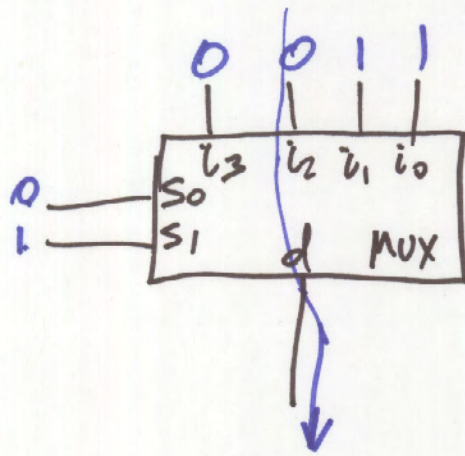



# EC6R 2181 - Extra Notes 10/26/09

(1)



$s_1$	$s_0$	$d$
0	0	$i_0$
0	1	$i_1$
1	0	$i_2$
1	1	$i_3$


if  
 $s_1, s_0 = 10$   
 $d = i_2$

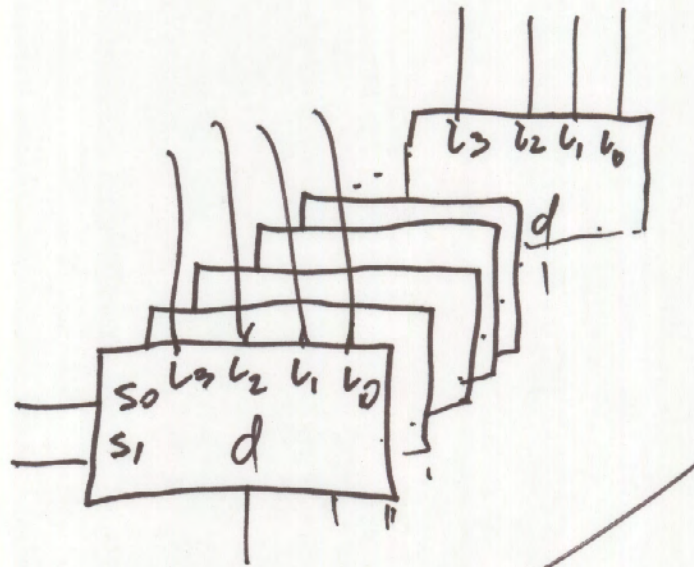


8 Muxes

Control - Controls all data bits  
 The same way

data - one mux per bit

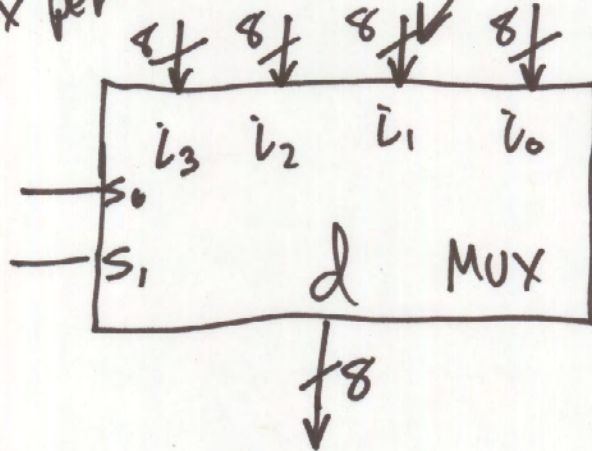

# ECGR2181 - Extra Notes - 10/26/09

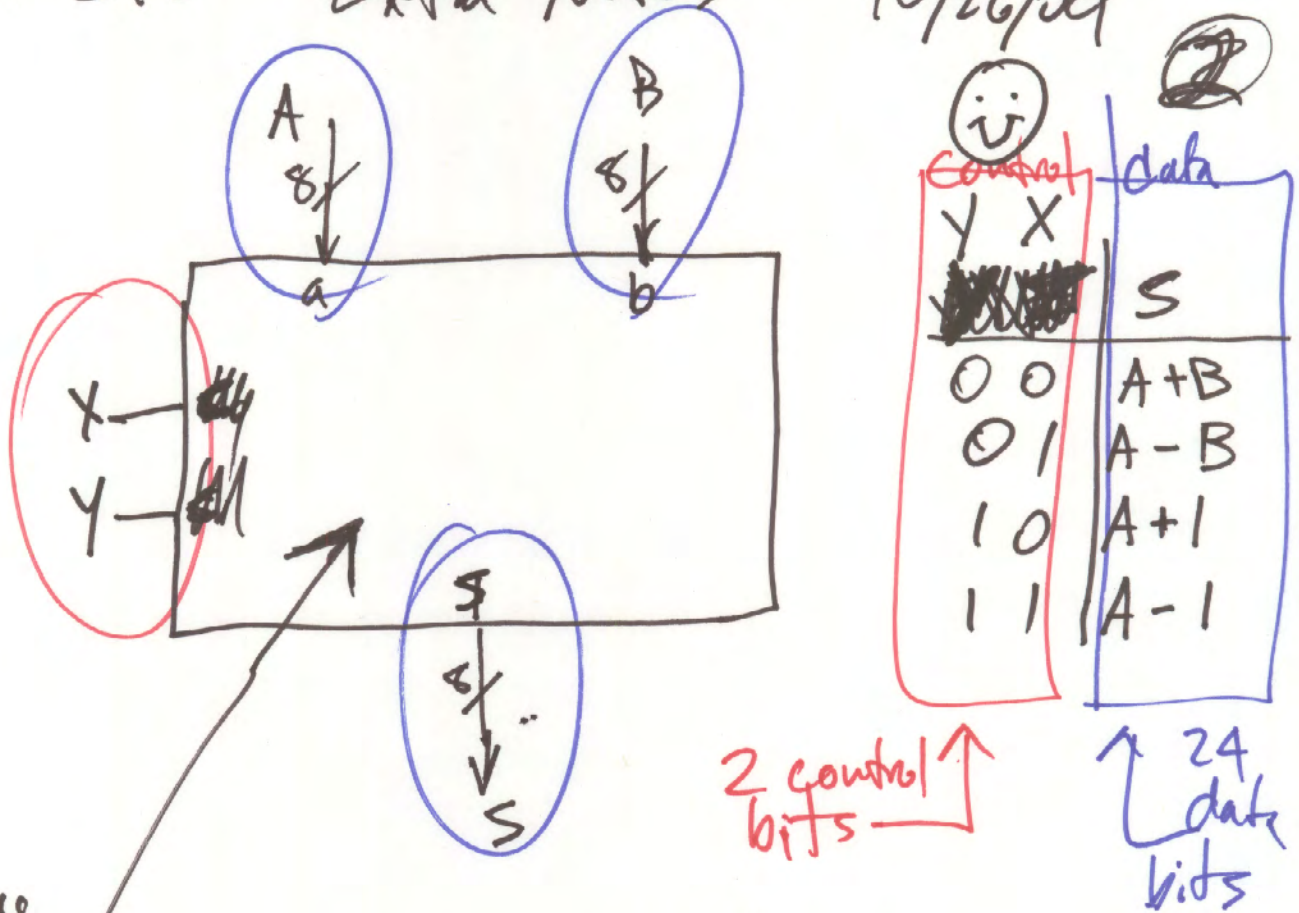


Inside

1) Adder (Cin)


2) Mux

3) Invert

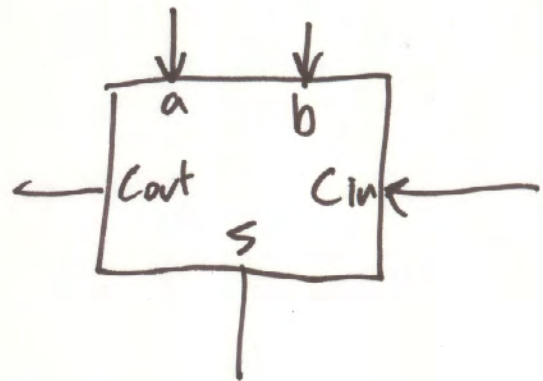

Pows Truth table

$2^n$   $n = \text{input bits}$

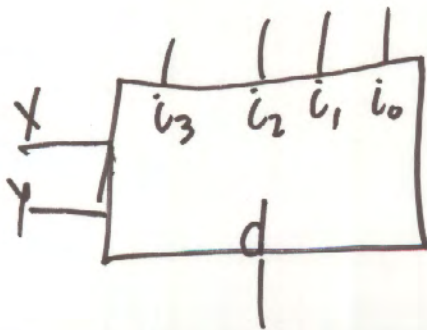

Y	X	d
0	0	$i_0$
0	1	$i_1$
1	0	$i_2$
1	1	$i_3$


a	b	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# ECGR2181 - Extra Notes 10/26/09 (3)

Y Y	S
00	A+B
01	A-B
10	A+1
11	A-1

What goes into the B input of the adder


B		C <sub>in</sub> = 0
~B		C <sub>in</sub> = 1
0000	0000	C <sub>in</sub> = 1
1111	1111	C <sub>in</sub> = 0

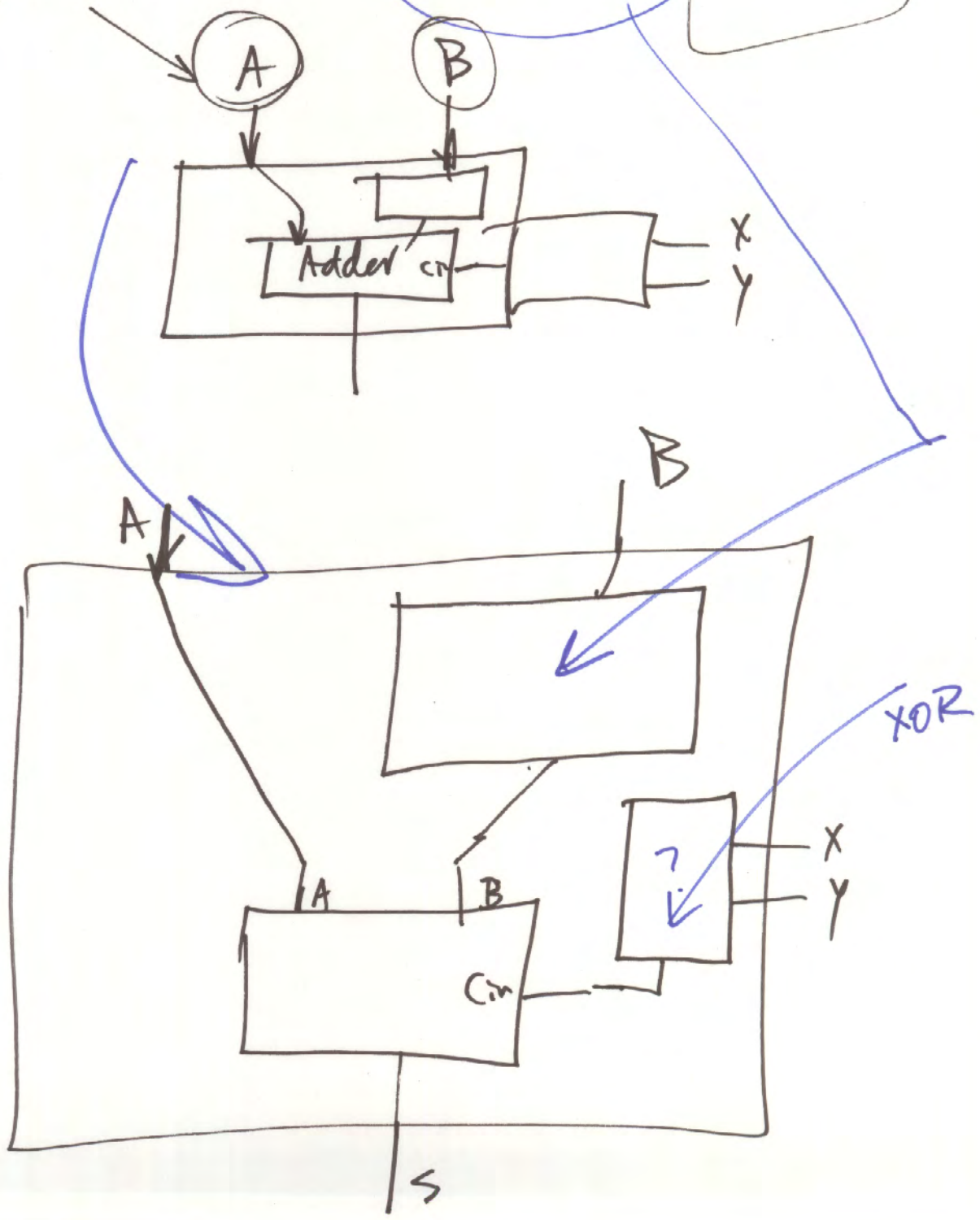

# ECGR 2181 - Extra Notes

10/26/09

④

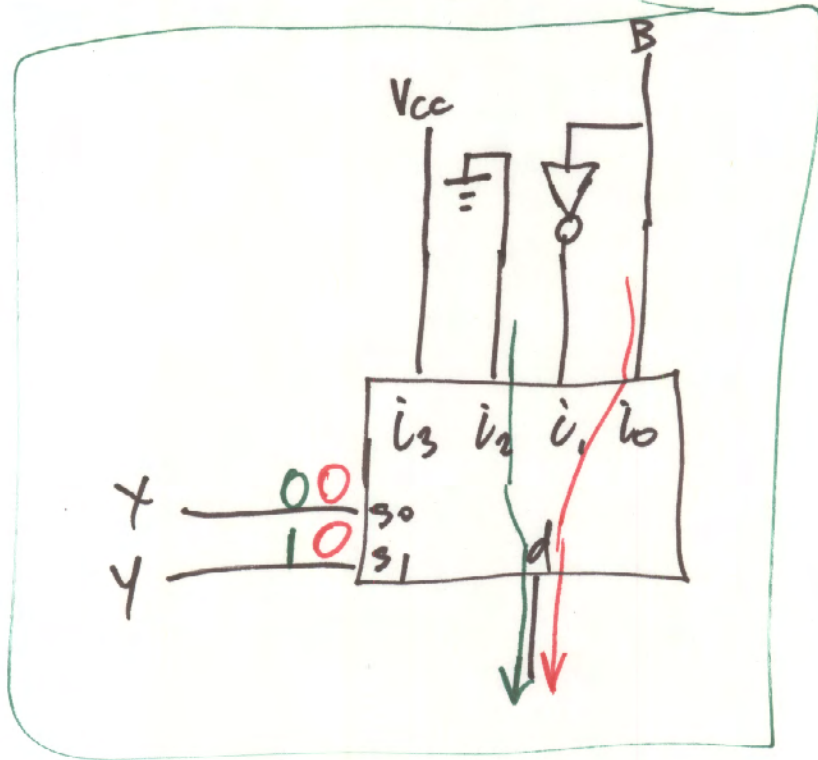

Y	X	$d_i$
0	0	$B_i$
0	1	$B_i$
1	0	0
1	1	1