

Digital Logic

2015-09-29


Solve a:

	yz	00	01	11	10
wx	00	1	0	1	1
	01	0	1	0	0
	11	1	0	1	1
	10	1	1	0	1

①

$$F(a) = XY + X'Z' + W'Y + WZ' + WX'Y' + W'XZ$$

Lab 2

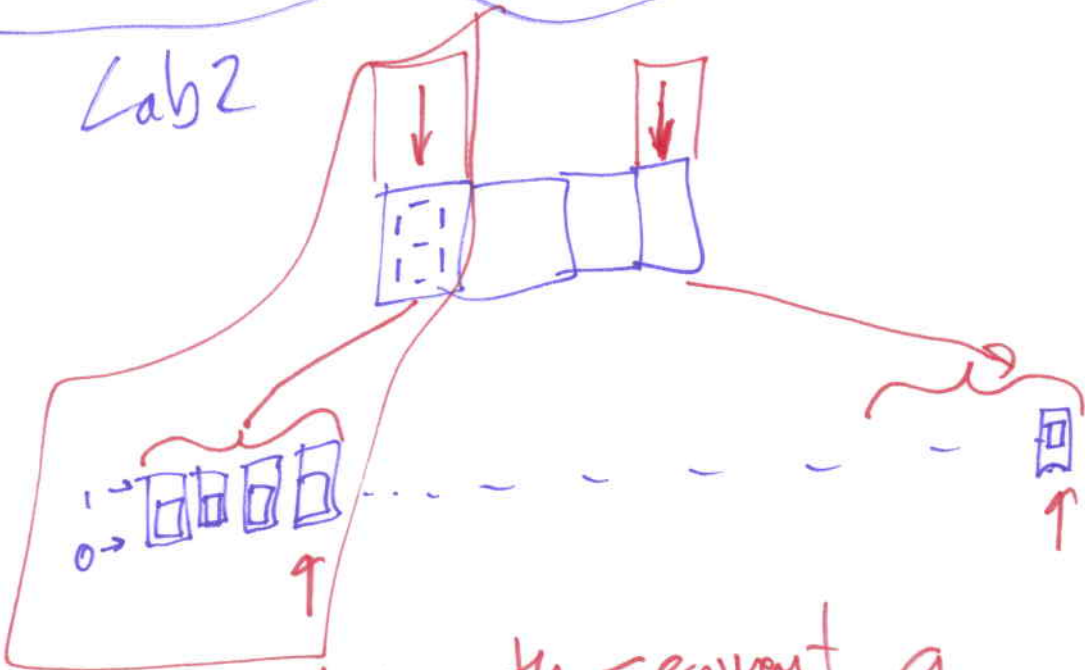

1. Start with sequant a
hex values 0, 2, 3, 5, 6, 7, 8, 9, A, C, E, F.